

Overvoltage Protection for the ADG5XXA Multiplexer Series

by Dan Sheehan

The ADG5XXA* multiplexer series is a family of single 8/16 channel and dual 4/8 channel parts. They are available in both latched (ADG52XA) and unlatched (ADG50XA) versions. These are high performance multiplexers that offer the following notable features: specifications for both single and dual supply operation, 1nA max leakage current, 200ns max turn-on and turn-off times and TTL compatibility with reduced single or dual supplies down to 5V.

The multiplexers are specified to operate with an analog input signal range within the supply rails, i.e., $V_{SS} \leq V_S (V_D) \leq V_{DD}$. The parts are not internally overvoltage protected (i.e., with resistors) to allow $V_S (V_D)$ to exceed the power supply rails. Thus, the ADG5XXA series, without external overvoltage protection, is best suited for use in systems where the analog input signals come from sources within the system, such as from op amps powered from the same supplies as the multiplexers.

However, in many applications such as process control systems, the analog input signals can originate from sources external to the system which contains the multiplexer. This can be potentially destructive to the multiplexer for two principal reasons:

1. The multiplexer power supplies may be turned off while the analog signals are still present.
2. The signal lines may receive induced voltage spikes which exceed the supplies to the multiplexer.

This application note addresses the above problems and outlines the protection circuitry required to allow the analog input signals to exceed the supply rails over the -40°C to $+85^{\circ}\text{C}$ temperature range.

OVERVOLTAGE PROTECTION: WHY?

The following is a brief and simplified analysis of what happens when a signal applied to the S(D) input of the multiplexer exceeds the power supply rails. The results outlined apply equally with the power supply rails at $\pm 15\text{V}$ or GND.

The basic CMOS switch consists of an n-channel MOSFET in parallel with a p-channel MOSFET. This structure which yields an excellent analog switch contains p-n junctions between the signal path and power supplies. These p-n junctions or diodes are reverse biased under normal operating conditions, i.e., $V_{SS} \leq V_S (V_D) \leq V_{DD}$. However, if $V_S (V_D)$ exceeds either power supply rail by approximately 0.7V, the normally reverse biased junctions will become forward biased. This means that with an analog input overvoltage, the S(D) input of the multiplexer will appear as a diode connected to the relevant power supply voltage. Therefore, $V_S (V_D)$ is clamped to a maximum of 0.7V greater than either supply rail and large currents can flow that will destroy the parts unless restricted. The simplest form of protection uses resistors in series with the S (D) inputs to limit the input current to safe levels.

PROTECTING TYPICAL MULTIPLEXER APPLICATION CIRCUITS

This section shows two typical multiplexer application circuits and outlines the operating conditions and protection circuitry required for the safe operation of the parts with an overvoltage on the analog inputs. The ADG506A is shown in both circuits but the same conditions and results apply to any part in ADG5XXA series.

Generic Multiplexer Circuit

Figure 1 shows the general use of a multiplexer. R1–R16 ($2.7\text{k}\Omega$) provide overvoltage protection.

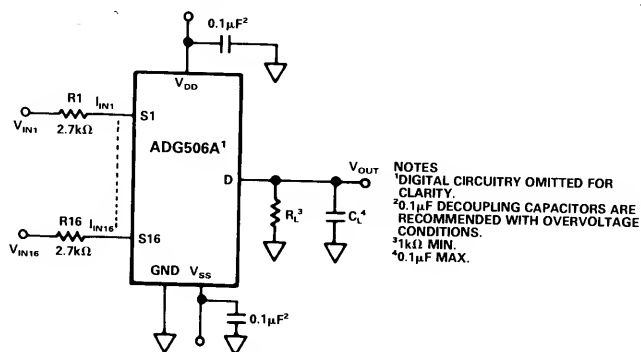


Figure 1. ADG506A Multiplexer Circuit

*ADG506A/ADG507A, ADG508A/ADG509A,
 ADG526A/ADG527A, ADG528A/ADG529A.

*TransZorb is a trademark of General Semiconductor Industries, Inc.